

Course Number	COE 328
Course Title	Digital Systems
Semester/Year	Semester 3, Year 2
Section Number	1

Lab 3 - Adder and Subtractor Unit

Assignment Title	Lab 3
Submission Date	October 19th, 2022
Due Date	October 23th, 2022

Student Name	Student ID (xxxx1234)	Signature*
Ahmad Najafi	24585	Najafi
Syed Maisam Abbas	03255	Maisam

(Note: Remove the first 4 digits from your student ID)

**By signing above you attest that you have contributed to this submission and confirm that all work you have contributed to this submission is your own work. Any suspicion of copying or plagiarism in this work will result in an investigation of Academic Misconduct and may result in a "0" on the work, an "F" in the course, or possibly more severe penalties, as well as a Disciplinary Notice on your academic record under the Student Code of Academic Conduct, which can be found online at: <http://www.ryerson.ca/senate/policies/pol60.pdf>.*

Figure 1: Block diagram of combined ASU 1

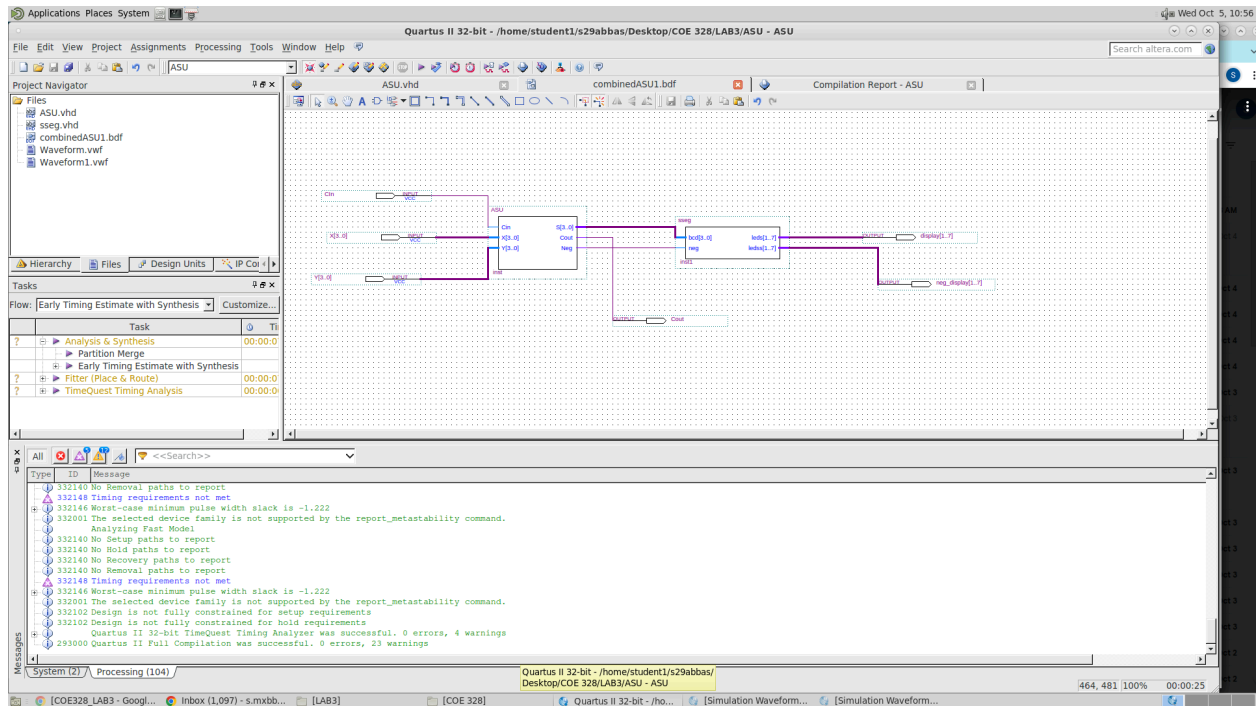


Figure 2: Simulation results of combined ASU 1

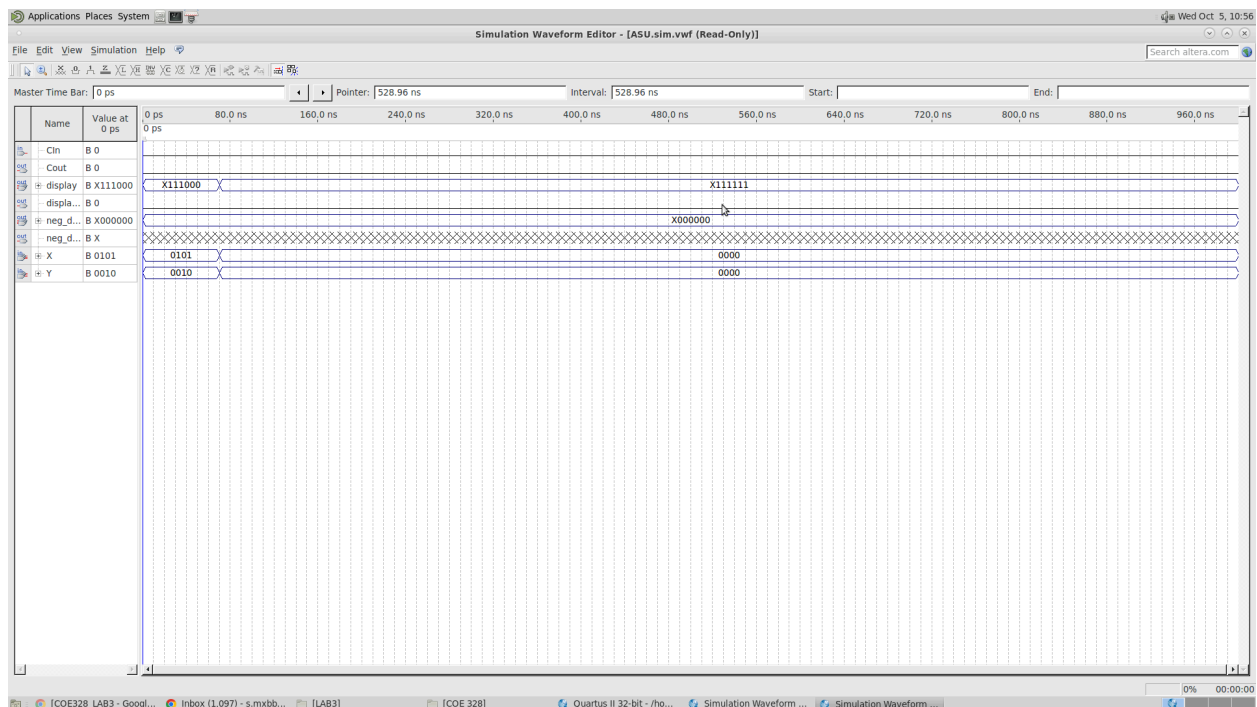


Figure 3: Simulation results of C

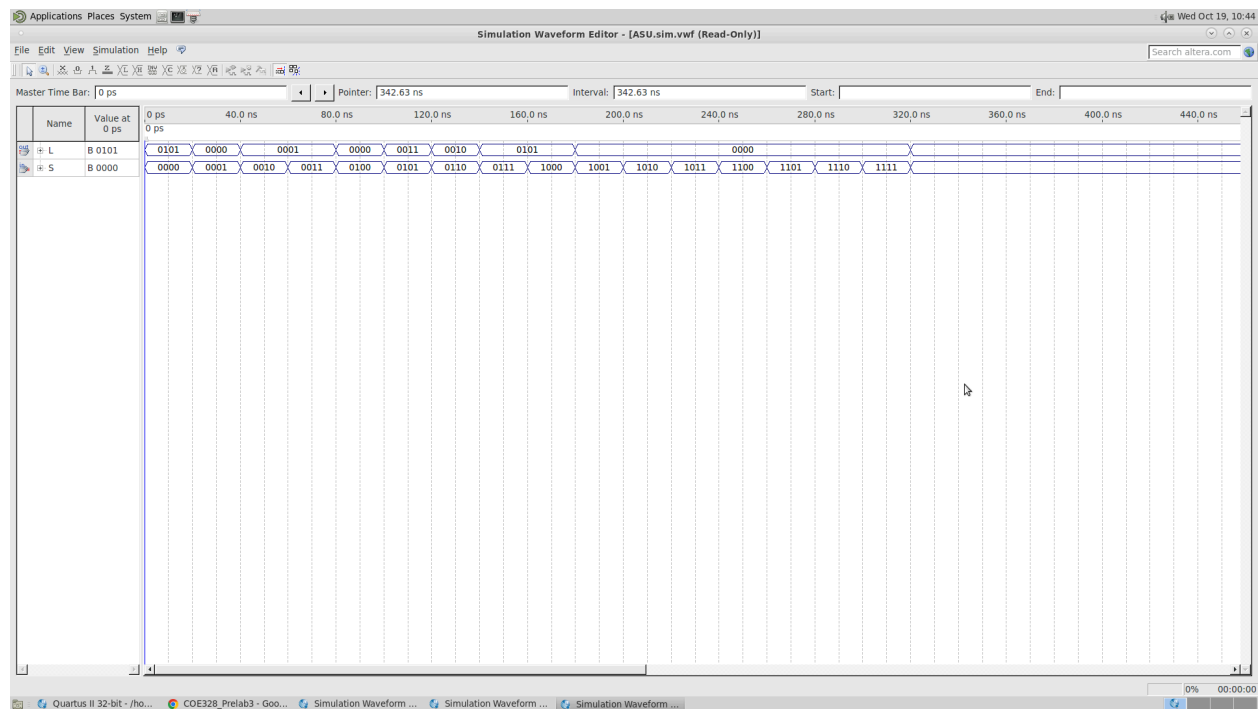


Figure 4: Block diagram of combined ASU 2

